


assignment 6

cj-prob2065.problem

Due date: Fri Feb 27 11:59:59 pm 2026 (EST)

Determine the equivalent resistance between the points A and B for group resistors in the drawing if $R_1 = 19.0 \, \Omega$, $R_2 = 3.5 \, \Omega$, $R_3 = 9.1 \, \Omega$, $R_4 = 7.0 \, \Omega$, $R_5 = 3.0 \, \Omega$, and $R_6 = 5.4 \, \Omega$.

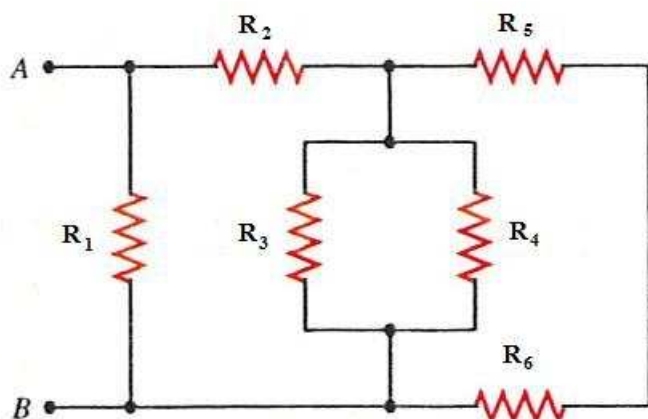You are correct. Your receipt no. is 163-1477




Kirchhoff, resistor circuit

None of the resistors in the circuit shown in the drawing are connected in series or in parallel with one another. $R_1 = 4.4 \, \Omega$, and $R_5 = 2.9 \, \Omega$. Find the current I_5 .

Incorrect.

Tries 1/10

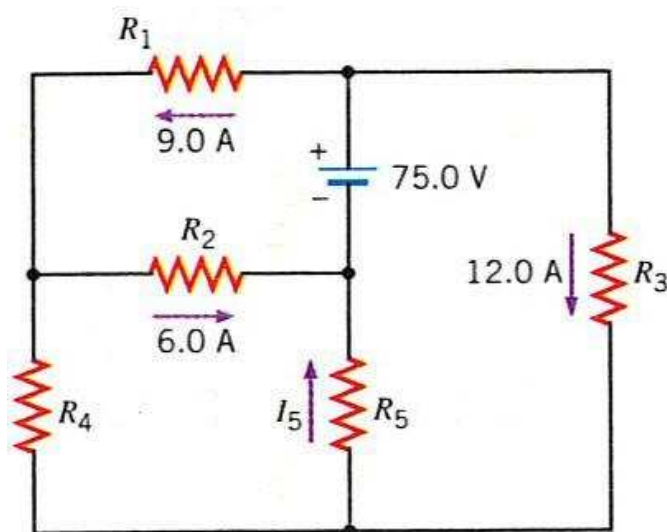

What is the resistance R_2 ?

Incorrect.

Tries 1/10

What is the resistance R_3 ?


Tries 0/10

sf-prob1826a.problem

Determine the magnitude of the potential difference, V_{ab} , for the circuit in the figure below. Note that each battery has an internal resistance, $R_1 = 1.90 \, \Omega$, $R_2 = 7.90 \, \Omega$, $R_3 = 2.90 \, \Omega$, $R_4 = 5.30 \, \Omega$, $R_5 = 6.00 \, \Omega$, $R_6 = 4.10 \, \Omega$ and $R_7 = 1.40 \, \Omega$. Assume that $\mathcal{E}_1 = 19.0 \, \text{V}$ and $\mathcal{E}_4 = 12.0 \, \text{V}$ and $\mathcal{E}_6 = 34.0 \, \text{V}$, as indicated in the figure.

Incompatible units. No conversion found between "ohm" and the required units.

Tries 0/10

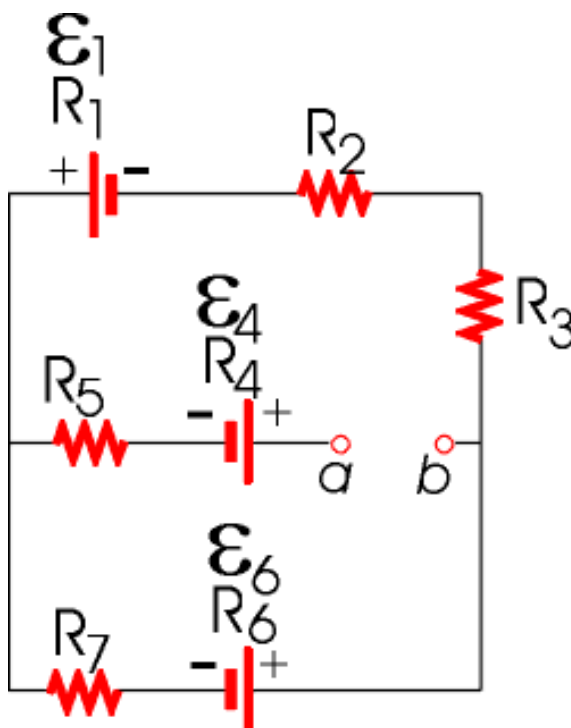

If points a and b are connected by a $R_8 = 6.90 \, \Omega$ resistor, what is the magnitude of the current through this resistor?


Incompatible units. No conversion found between "ohm" and the required units.

Tries 0/10

sf-prob1822.problem

Four resistors, $R_1 = 33.0 \, \Omega$, $R_2 = 51.0 \, \Omega$, $R_3 = 86.0 \, \Omega$ and $R_4 = 17.0 \, \Omega$, are connected to a battery with a terminal voltage of $12.0 \, \text{V}$, as shown in the figure below. Determine the power dissipated in the $R_2 = 51.0 \, \Omega$ resistor.


Tries 0/10

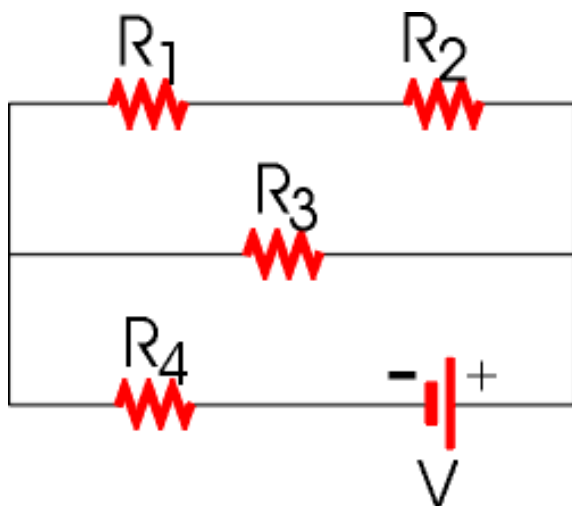

sb-prob2814.problem


The power delivered to the top part of the circuit shown below does not depend on whether the switch is opened or closed. If $R=1.17\Omega$, what is R' ? Neglect the internal resistance of the voltage source.

Tries 0/10

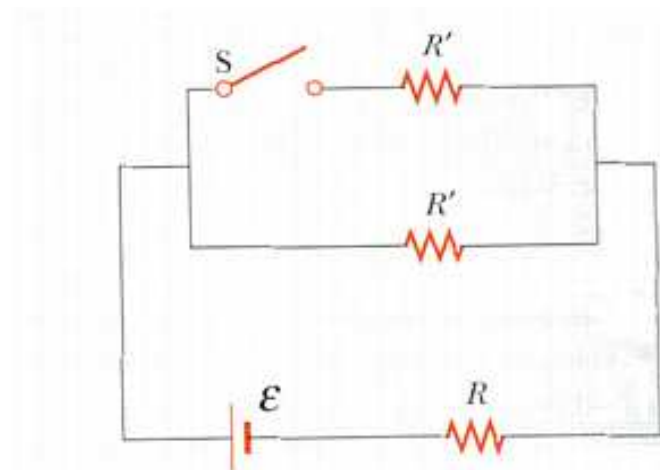

sb-prob2818a.problem

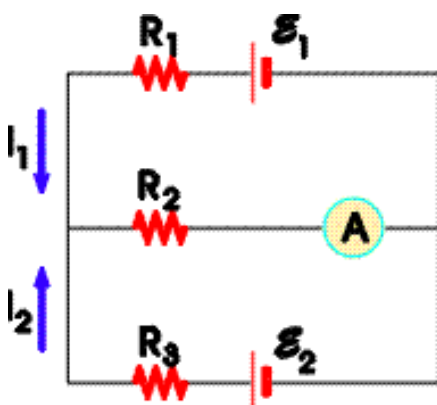The ammeter shown in the figure below, reads 1.89A. $\mathcal{E}_1=18.0\text{V}$, $R_1=6.00\Omega$, $R_2=4.00\Omega$ and $R_3=2.00\Omega$.



Calculate I_1 .

Tries 0/10

Calculate I_2 .

Tries 0/10

Calculate \mathcal{E}_2 .

Tries 0/10

sb-prob2816.problem


7. Two resistors connected in series have an equivalent resistance of 730Ω . When they are connected in parallel, their equivalent resistance is 139Ω . Calculate the resistance of each resistor. Enter the smaller one first.

Tries 0/10

sb-prob2822a.problem

8a. Using Kirchhoff's rules, calculate the current I_1 in resistor R_1 , using the directions indicated in the figure below. Assume that $R_1 = 3.00\text{k}\Omega$, $R_2 = 5.00\text{k}\Omega$, $R_3 = 7.00\text{k}\Omega$, $\mathcal{E}_1 = 80.0\text{V}$, $\mathcal{E}_2 = 70.0\text{V}$ and $\mathcal{E}_3 = 95.0\text{V}$.

Tries 0/10

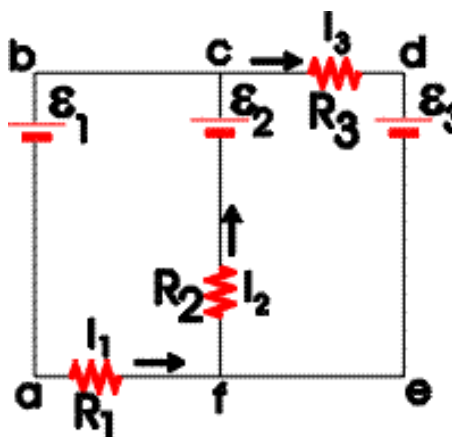

8b. Calculate the current I_2 , in resistor R_2 , using the directions shown.

Tries 0/10

8c. Calculate the current I_3 , in resistor R_3 , using the directions shown.

Tries 0/10

8d. Calculate the magnitude of the potential difference between points c and f.


Tries 0/10

sb-prob2823.problem

If $R=1.33\text{E}+3\Omega$ and $\epsilon=215\text{V}$, determine the magnitude of the current in the horizontal wire between a and e.

Assignments

Tries 0/10

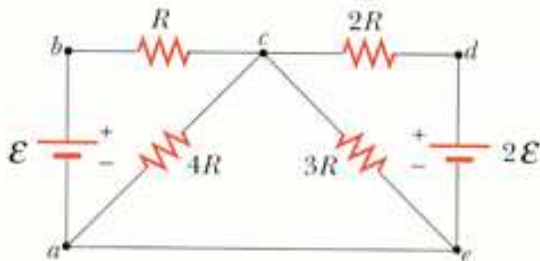

sb-prob2830a.problem

A 2.03nF capacitor with an initial charge of 5.28uC is discharged through a $1.18\text{k}\Omega$ resistor. Calculate the current through the resistor 7.40us after the resistor is connected across the terminals of the capacitor.

Tries 0/10

What charge remains on the capacitor after 6.40us ?

Tries 0/10


What is the maximum current in the resistor?

Tries 0/10

sb-prob2853.problem

Calculate the magnitude of the potential difference between points a and b in the figure if $R_1=2.27\Omega$, $R_2=4.42\Omega$, and $R_3=10.00\Omega$.

Tries 0/10

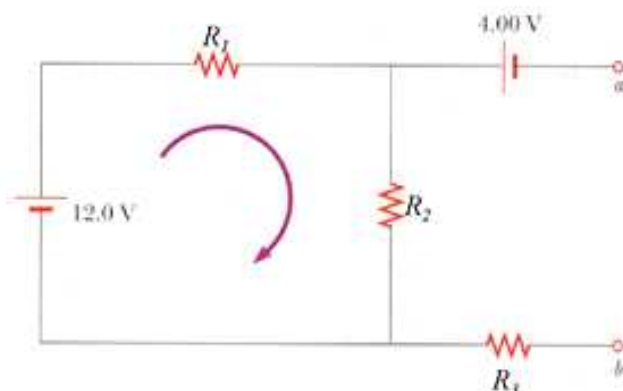

sb-prob2852.problem

A battery has an emf of 8.38V and an internal resistance of 1.10Ω . What resistance connected across the battery will absorb from it a power of 11.6W ? Enter both of the two possible answers, the larger one first.

Tries 0/10


sb-prob2854.problem

A $1.40\text{E-}5\text{F}$ capacitor is charged by a 10.0V battery through a resistance R . The capacitor reaches a potential difference of 4.84V at a time 2.23s after charging begins. Find R .

Tries 0/10

sb-prob2872a.problem

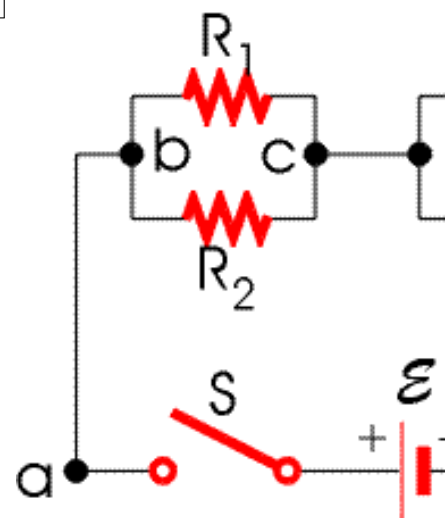The circuit in the figure below contains two resistors, $R_1 = 4.00\text{k}\Omega$ and $R_2 = 5.00\text{k}\Omega$, and two capacitors, $C_1 = 4.00\text{uF}$ and $C_2 = 5.00\text{uF}$, connected to a battery with emf $\mathcal{E} = 100\text{V}$. If no charges exist on the capacitors before switch S is closed, determine the charge q_1 on capacitor C_1 1.00ms after the switch is closed.



Tries 0/10

Determine the charge q_2 on capacitor C_2 1.00ms after the switch is closed.

Tries 0/10